

3.6 KOPLINGER MED USYMETRISKE ENERGIKILDER

3.6.1

$$a) \quad I \quad \bar{I}_1 \cdot R_{i1} + I \cdot R_y = E_1 \quad \bar{I} = \bar{I}_1 + \bar{I}_2$$

$$II \quad \bar{I}_2 \cdot R_{i2} + I \cdot R_y = E_2$$

$$I \quad \bar{I}_1 \cdot R_{i1} + \bar{I}_1 \cdot R_y + \bar{I}_2 \cdot R_y = E_1$$

$$II \quad \bar{I}_2 \cdot R_{i2} + \bar{I}_1 \cdot R_y + \bar{I}_2 \cdot R_y = E_2$$

$$I \quad \bar{I}_1 \cdot 10\Omega + \bar{I}_1 \cdot 50\Omega + \bar{I}_2 \cdot 50\Omega = 230V$$

$$II \quad \bar{I}_2 \cdot 13\Omega + \bar{I}_1 \cdot 50\Omega + \bar{I}_2 \cdot 50\Omega = 200V$$

$$I \quad \bar{I}_1 \cdot 60\Omega + \bar{I}_2 \cdot 50\Omega = 230V \quad | \cdot 5$$

$$II \quad \bar{I}_1 \cdot 50\Omega + \bar{I}_2 \cdot 63\Omega = 200V \quad | \cdot (-6)$$

$$I \quad \bar{I}_1 \cdot 300\Omega + \bar{I}_2 \cdot 250\Omega = 1150V$$

$$II \quad -\bar{I}_2 \cdot 300\Omega - \bar{I}_2 \cdot 378\Omega = -1200V$$

$$-\bar{I}_2 \cdot 128\Omega = -50V$$

$$\bar{I}_2 = \frac{-50V}{-128\Omega} = \underline{\underline{0,390A}}$$

$$I \quad \bar{I}_1 \cdot 300\Omega + \bar{I}_2 \cdot 250\Omega = 1150V$$

$$\bar{I}_1 \cdot 300\Omega + 0,390A \cdot 250\Omega = 1150V$$

$$\bar{I}_1 = \frac{1150V - (0,390A \cdot 250\Omega)}{300\Omega} = \underline{\underline{3,51A}}$$

$$I = \bar{I}_1 + \bar{I}_2 = 0,390A + 3,51A = \underline{\underline{3,90A}} \quad b) \quad U = I \cdot R_y = 3,90A \cdot 50\Omega = \underline{\underline{194,9V}}$$

3.6.2

$$\text{I} \quad I_1 \cdot R_1 + I_1 \cdot R_3 + I_2 \cdot R_3 + I_1 \cdot R_2 = U_1$$

$$\text{II} \quad I_1 \cdot R_3 + I_2 \cdot R_3 + I_2 \cdot R_4 + I_2 \cdot R_5 = U_2$$

$$\text{I} \quad I_1 \cdot 100\Omega + I_1 \cdot 50\Omega + I_2 \cdot 50\Omega + I_1 \cdot 130\Omega = 130\text{V}$$

$$\text{II} \quad I_1 \cdot 50\Omega + I_2 \cdot 50\Omega + I_2 \cdot 100\Omega + I_2 \cdot 70\Omega = 110\text{V}$$

$$\text{I} \quad I_1 \cdot 280\Omega + I_2 \cdot 50\Omega = 130\text{V} \quad | \cdot 22$$

$$\text{II} \quad I_1 \cdot 50\Omega + I_2 \cdot 220\Omega = 110\text{V} \quad | \cdot (-5)$$

$$\text{I} \quad I_1 \cdot 6160\Omega + I_2 \cdot 1100\Omega = 2860\text{V}$$

$$\text{II} \quad -I_1 \cdot 250\Omega - I_2 \cdot 1100\Omega = -550\text{V}$$

$$\text{I} \quad I_1 \cdot 5910\Omega = 2310\text{V}$$

$$I_1 = \frac{2310\text{V}}{5910\Omega} = \underline{\underline{0,391\text{A}}}$$

$$\text{I} \quad I_1 \cdot 280\Omega + I_2 \cdot 50\Omega = 130\text{V}$$

$$0,391\text{A} \cdot 280\Omega + I_2 \cdot 50\Omega = 130\text{V}$$

$$I_2 = \frac{130\text{V} - (0,391\text{A} \cdot 280\Omega)}{50\Omega} = \underline{\underline{0,411\text{A}}}$$

$$I = I_1 + I_2 = 0,391\text{A} + 0,411\text{A} = \underline{\underline{0,802\text{A}}}$$

b)

$$U = I \cdot R_3 = 0,802\text{A} \cdot 50\Omega = \underline{\underline{40,1\text{V}}}$$

3.6.3

$$a) \quad I \quad I_1 \cdot R_1 + I_1 \cdot R_2 + I_1 \cdot R_y + I_2 \cdot R_y + I_1 \cdot R_6 = U_1 + (-U_2)$$

$$II \quad I_2 \cdot R_3 + I_1 \cdot R_y + I_2 \cdot R_y + I_2 \cdot R_5 + I_2 \cdot R_4 = U_3$$

$$I \quad I_1 \cdot 70\Omega + I_1 \cdot 60\Omega + I_1 \cdot 100\Omega + I_2 \cdot 100\Omega + I_1 \cdot 70\Omega = 10V + (-12V)$$

$$II \quad I_2 \cdot 50\Omega + I_1 \cdot 100\Omega + I_2 \cdot 100\Omega + I_2 \cdot 50\Omega + I_2 \cdot 40\Omega = 14V$$

$$I \quad I_1 \cdot 300\Omega + I_2 \cdot 100\Omega = -2V$$

$$II \quad I_1 \cdot 100\Omega + I_2 \cdot 240\Omega = 14V \quad | \cdot (-3)$$

$$I \quad I_1 \cdot 300\Omega + I_2 \cdot 100\Omega = -2V$$

$$II \quad -I_1 \cdot 300\Omega - I_2 \cdot 720\Omega = -42V$$

$$-I_2 \cdot 620\Omega = -44V$$

$$I_2 = \underline{\underline{0,0710A}} = \underline{\underline{71,0mA}}$$

$$I \quad I_1 \cdot 300\Omega + I_2 \cdot 100\Omega = -2V$$

$$I_1 \cdot 300\Omega + 0,071A \cdot 100\Omega = -2V$$

$$I_1 = \frac{-2V - (0,071A \cdot 100\Omega)}{300\Omega} = \underline{\underline{\div 0,0303A}} = \underline{\underline{\div 30,3mA}}$$

$$I = I_1 + I_2 = -30,3 \cdot 10^{-3}A + 71,0 \cdot 10^{-3}A = \underline{\underline{0,0406A}} = \underline{\underline{40,6mA}}$$

$$b) \quad U = I \cdot R_y = 40,6 \cdot 10^{-3}A \cdot 100\Omega = \underline{\underline{4,06V}}$$

3.6.4

$$a) \quad U = U \quad \bar{I} = \bar{I}_1 + \bar{I}_2$$

$$E_1 - \Delta U_{i1} = E_2 - \Delta U_{i2} \quad \bar{I}_2 = I - \bar{I}_1$$

$$E_1 - \bar{I}_1 \cdot R_{i1} = E_2 - \bar{I}_2 \cdot R_{i2}$$

$$100\text{V} - \bar{I}_1 \cdot 0,2\Omega = 102\text{V} - \bar{I}_2 \cdot 0,2\Omega$$

$$100\text{V} - \bar{I}_1 \cdot 0,2\Omega = 102\text{V} - (I - \bar{I}_1) \cdot 0,2\Omega$$

$$100\text{V} - \bar{I}_1 \cdot 0,2\Omega = 102\text{V} - 2\text{A} \cdot 0,2\Omega + \bar{I}_1 \cdot 0,2\Omega$$

$$- \bar{I}_1 \cdot 0,2\Omega - \bar{I}_1 \cdot 0,2\Omega = 102\text{V} - 100\text{V} - 0,4\text{V}$$


$$\bar{I}_1 \cdot 0,4\Omega = -1,6\text{V}$$

$$\bar{I}_1 = \frac{-1,6\text{V}}{0,4\Omega} = \underline{\underline{-4\text{A}}}$$

$$\bar{I}_2 = I - \bar{I}_1 = 2\text{A} - (-4\text{A}) = \underline{\underline{6\text{A}}}$$

$$b) \quad U = E_1 - I_1 \cdot R_{i1} = 100\text{V} - (-4\text{A} \cdot 0,2\Omega) = \underline{\underline{100,8\text{V}}}$$
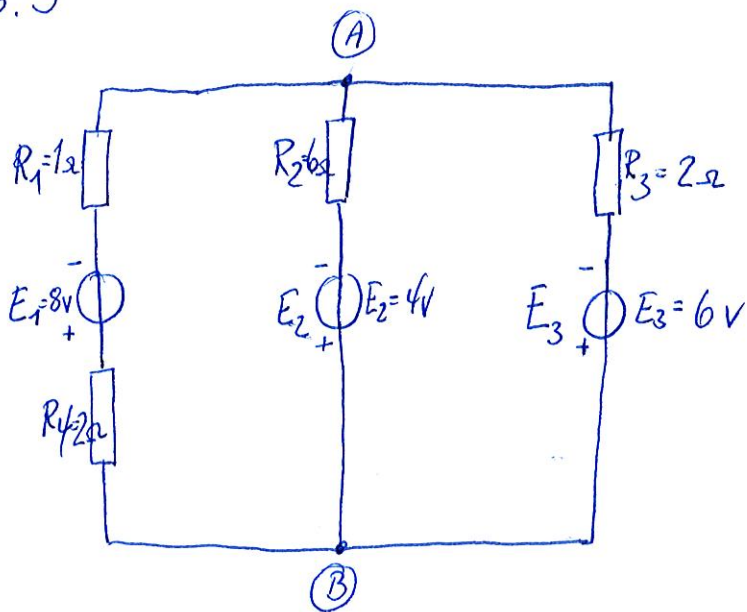
$$R_y = \frac{U}{I} = \frac{100,8\text{V}}{2\text{A}} = \underline{\underline{50,4\Omega}}$$



Finu Strømmene i kretsen

Antatt strømretning fra pluss på polene til spenningskildene.

Tilfelle 1 E_2 og E_3 kortsluttet

$$I_{11} = \frac{E_1}{R_1 + R_4 + \frac{R_2 + R_3}{R_2 + R_3}} = \frac{8V}{1\Omega + 2\Omega + \frac{6\Omega + 2\Omega}{6\Omega + 2\Omega}} = 1,778A \quad \text{opp}$$

$$V_{AB1} = E_1 - \Delta U_{R_{12}} = -(I_{11} \cdot R_1 + I_{11} \cdot R_4) = 8V - (1,778A \cdot 1\Omega + 1,778A \cdot 2\Omega)$$

$$V_{AB1} = 2,667V$$

$$I_{21} = \frac{V_{AB1}}{R_2} = \frac{2,667V}{6\Omega} = 0,444A \quad \text{ned}$$

$$I_{31} = \frac{V_{AB1}}{R_3} = \frac{2,667V}{2\Omega} = 1,333A \quad \text{ned}$$

Tilfelle 2 E_1 og E_2 kortsluttet

$$I_{22} = \frac{E_2}{R_2 + \frac{R_3 \cdot (R_1 + R_4)}{R_3 + (R_1 + R_4)}} = \frac{4V}{6\Omega + \frac{2\Omega \cdot (1\Omega + 2\Omega)}{2\Omega + (1\Omega + 2\Omega)}} = 0,555A \quad \text{opp}$$

$$V_{AB2} = E_2 - \Delta U_{R_2} = E_2 - I_{22} \cdot R_2 = 4V - 0,555A \cdot 6\Omega = 0,6667V$$

$$I_{12} = \frac{V_{AB2}}{R_1 + R_4} = \frac{0,6667V}{1\Omega + 2\Omega} = 0,222A \quad \text{ned}$$

$$I_{32} = \frac{V_{AB2}}{R_3} = \frac{0,6667V}{2\Omega} = 0,333A \quad \text{ned}$$

Tilfelle 3 E_1 og E_2 kortsluttet

$$I_{33} = \frac{E_3}{R_3 + \frac{R_2 \cdot (R_1 + R_4)}{R_2 + (R_1 + R_4)}} = \frac{6V}{2\Omega + \frac{6\Omega \cdot (1\Omega + 2\Omega)}{6\Omega + (1\Omega + 2\Omega)}} = \underline{1,5A} \text{ (OPP)}$$

$$U_{AB3} = E_3 - \Delta U_{R_3} = E_3 - I_{33} \cdot R_3 = 6V - 1,5A \cdot 2\Omega = \underline{3,0V}$$

$$I_{13} = \frac{U_{AB3}}{R_1 + R_4} = \frac{3,0V}{1\Omega + 2\Omega} = \underline{1,0A} \text{ (ned)}$$

$$I_{23} = \frac{U_{AB3}}{R_2} = \frac{3,0V}{6\Omega} = \underline{0,5A} \text{ (ned)}$$

$$I_1 = \overset{\text{(OPP)}}{I_{11}} - \overset{\text{(ned)}}{I_{12}} - \overset{\text{(ned)}}{I_{13}} = 1,778A - 0,222A - 1,0A = \underline{\underline{0,555A}}$$

$$I_2 = I_{22} - I_{21} - I_{23} = 0,555A - 0,444A - 0,5A = \underline{\underline{-0,389A}}$$

$$I_3 = I_{33} - I_{31} - I_{32} = 1,5A - 1,333A - 0,333A = \underline{\underline{-0,166A}}$$