

## 8.0 FLERFASSET VEKSELSTRØM

## 8.1 TREFASET VEKSELSTRØM I SYMMETRI

27

## 8.1.1

a) Stjernekopling  
 $U = 230V, 50Hz$

$$I_f = I = \underline{10A}$$

$$I = 10A$$

$$U_f = \frac{U}{\sqrt{3}} = \frac{230V}{\sqrt{3}} = \underline{132,8V}$$

b)

$$P = \sqrt{3} \cdot U \cdot I \cdot \cos \varphi = \sqrt{3} \cdot 230V \cdot 10A \cdot \cos 0^\circ = \underline{3984W}$$

## 8.1.2

a) Trekantkopling  
 $U = 400V, 50Hz$

$$I_f = \frac{I}{\sqrt{3}} = \frac{5A}{\sqrt{3}} = \underline{2,89A}$$


$$I = 5A$$

$$U_f = U = \underline{400V}$$


b)

$$P = \sqrt{3} \cdot U \cdot I \cdot \cos \varphi = \sqrt{3} \cdot 400V \cdot 5A = \underline{3464W}$$

## 8.1.4

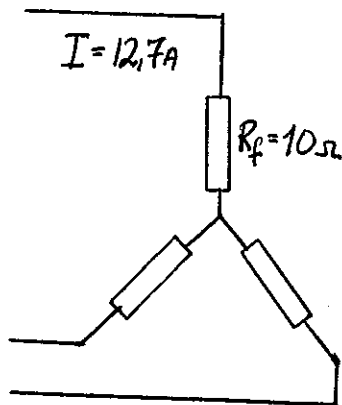

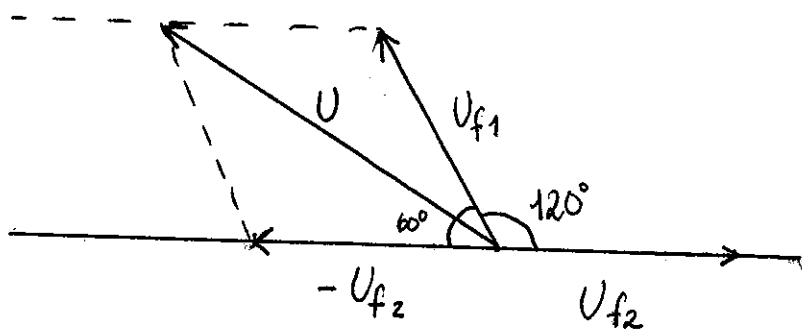
a)  $U_f = I_f \cdot R_f = 12,7A \cdot 10\Omega = \underline{127V}$



b)  $U = U_f \cdot \sqrt{3} = 127V \cdot \sqrt{3} = \underline{220V}$

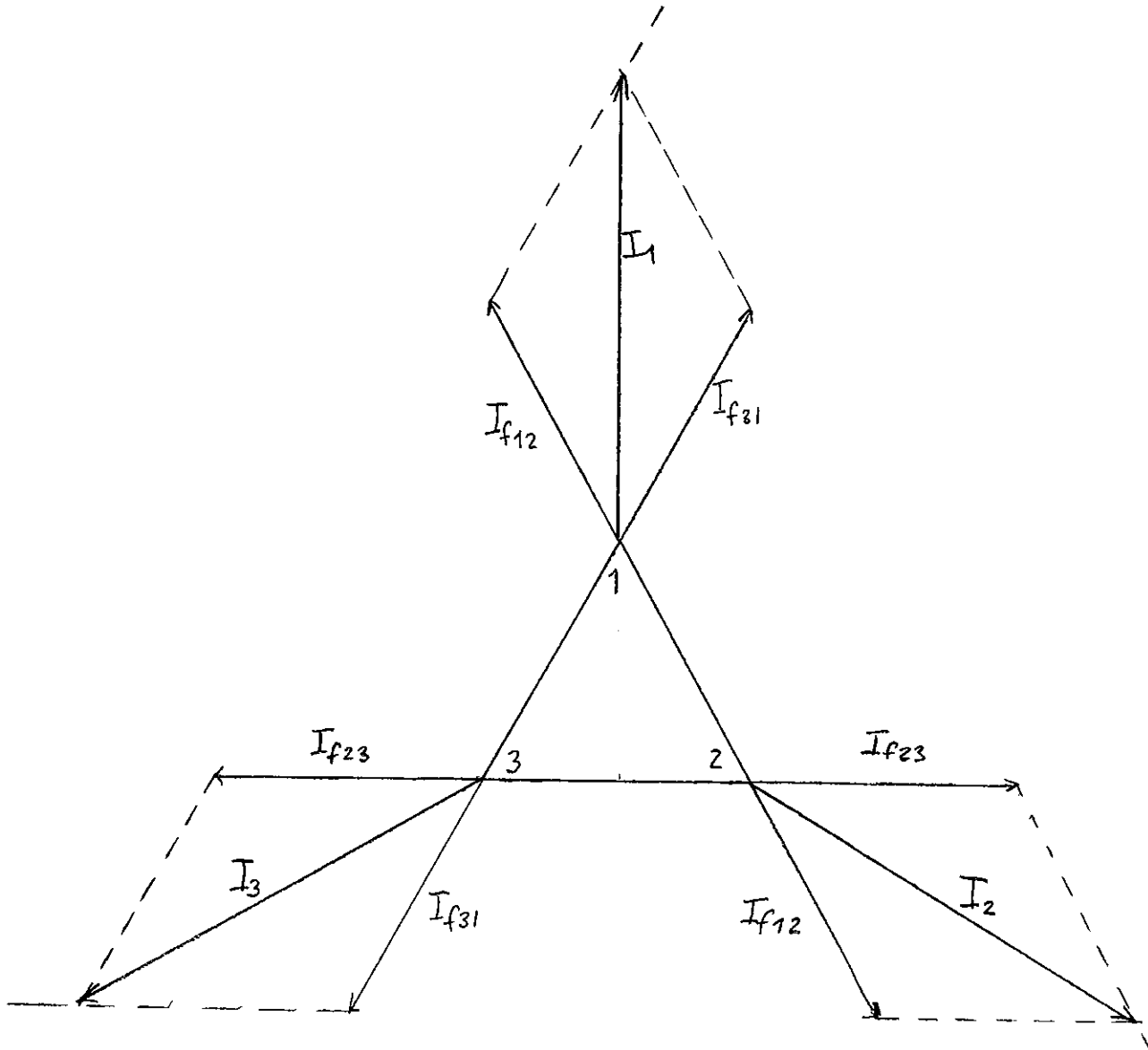8.1.5

$$a) I_f = \frac{U_f}{R_f} = \frac{400V}{20\Omega} = \underline{20A}$$



$$b) I_1 = I_f \cdot \sqrt{3} = 20A \cdot \sqrt{3} = \underline{\underline{34,64A}}$$

8.1.6

$$U = 240 \text{ V}, 50 \text{ Hz} \quad a) \quad U_f = \frac{U}{\sqrt{3}} = \frac{240 \text{ V}}{\sqrt{3}} = \underline{\underline{138,6 \text{ V}}}$$

$$\cos \phi = 0,85$$

$$I = 7 \text{ A}$$

Stjernekopling

$$b) \quad S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 240 \text{ V} \cdot 7 \text{ A} = \underline{\underline{2910 \text{ VA}}}$$

$$P = S \cdot \cos \phi = 2910 \text{ VA} \cdot 0,85 = \underline{\underline{2473 \text{ W}}}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{2910 \text{ VA}^2 - 2473 \text{ W}^2} = \underline{\underline{1533 \text{ VAR}}}$$

Stjernekopling:

$$c) \quad Z_f = \frac{U_f}{I_f} = \frac{138,6 \text{ V}}{7 \text{ A}} = \underline{\underline{19,8 \Omega}}$$

Trekanthkopling:

$$U_f = U_H = \underline{\underline{240 \text{ V}}}$$

$$I_f = \frac{U_f}{Z_f} = \frac{240 \text{ V}}{19,8 \Omega} = \underline{\underline{12,12 \text{ A}}}$$

$$d) \quad I = I_f \cdot \sqrt{3} = 12,12 \text{ A} \cdot \sqrt{3} = \underline{\underline{21,0 \text{ A}}}$$

$$S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 240 \text{ V} \cdot 21,0 \text{ A} = \underline{\underline{8729,5 \text{ VA}}}$$

$$P = S \cdot \cos \phi = 8729,5 \text{ VA} \cdot 0,85 = \underline{\underline{7420,1 \text{ W}}}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{8729,5 \text{ VA}^2 - 7420,1 \text{ W}^2} = \underline{\underline{4598,5 \text{ VAR}}}$$

e)

$$\frac{S_{\Delta}}{S_Y} = \frac{8729,5 \text{ VA}}{2910,0 \text{ VA}} = 3$$

$$\frac{I_{\Delta}}{I_Y} = \frac{21,0 \text{ A}}{7,0 \text{ A}} = 3$$


Effektene og Hovedstrømmen er tre ganger så stor i trekant som i stjerne.

8.1.7

$$a) S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 440V \cdot 7A = \underline{\underline{5334,7VA}}$$

$$P = \sqrt{3} \cdot U \cdot I \cdot \cos\phi = \sqrt{3} \cdot 440V \cdot 7A \cdot 0,7 = \underline{\underline{3734,3W}}$$
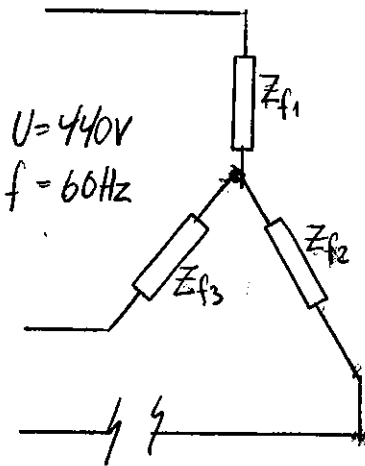
$$Q = \sqrt{S^2 - P^2} = \sqrt{5334,7VA^2 - 3734,3W^2} = \underline{\underline{3809,7VAR}}$$



b) Hel stjernekopling:

$$Z_f = \frac{U_f}{I_f} = \frac{\frac{U}{\sqrt{3}}}{I_f} = \frac{\frac{440V}{\sqrt{3}}}{12A} = \underline{\underline{21,17\Omega}}$$

$$I = \frac{U}{Z_{f1} + Z_{f2}} = \frac{440V}{21,17\Omega + 21,17\Omega} = \underline{\underline{10,3A}}$$

$$S = U \cdot I = 440V \cdot 10,3A = \underline{\underline{4572,6VA}}$$

$$P = U \cdot I \cdot \cos\phi = 440V \cdot 10,3A \cdot 0,7 = \underline{\underline{3200,8W}}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{4572,6VA^2 - 3200,8W^2} = \underline{\underline{3265,5VAR}}$$

c) Trekant


$$I_f = \frac{U_f}{Z_f} = \frac{440V}{21,17\Omega} = \underline{\underline{20,78A}} \quad I = I_f \cdot \sqrt{3} = 20,78A \cdot \sqrt{3} = \underline{\underline{36,0A}}$$

$$S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 440V \cdot 36,0A = \underline{\underline{27,44kVA}}$$

$$P = \sqrt{3} \cdot U \cdot I \cdot \cos\phi = \sqrt{3} \cdot 440V \cdot 36,0A \cdot 0,7 = \underline{\underline{19,21kW}}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{27,44 \cdot 10^3 VA^2 - 19,21 \cdot 10^3 W^2} = \underline{\underline{19,59kVAR}}$$

d)

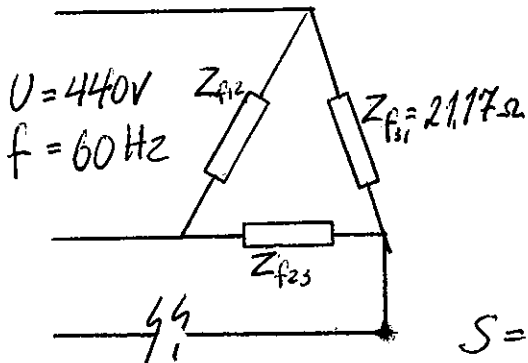

$$\frac{1}{Z} = \frac{1}{Z_{f12}} + \frac{1}{Z_{f23} + Z_{f31}} = \frac{1}{21,17\Omega} + \frac{1}{21,17\Omega + 21,17\Omega} = \underline{\underline{Z = 14,1\Omega}}$$

$$I = \frac{U}{Z} = \frac{440V}{14,1\Omega} = \underline{\underline{31,18A}}$$

$$S = U \cdot I = 440V \cdot 31,18A = \underline{\underline{13,72kVA}}$$

$$P = U \cdot I \cdot \cos\phi = 440V \cdot 31,18A \cdot 0,7 = \underline{\underline{9,60kW}}$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{13,72 \cdot 10^3 VA^2 - 9,60 \cdot 10^3 W^2} = \underline{\underline{9,80kVAR}}$$

8.1.8

STJERNEKOPLING:

$$a) S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 200V \cdot 12A = \underline{\underline{4157 VA}}$$

$$\cos \varphi = 0,85 \Rightarrow \varphi = 31,79^\circ$$

$$\bar{S} = S \angle \varphi = 4157VA \angle 31,79^\circ = \underline{\underline{3533W + j2190VAR}}$$

$$b) Z_f = \frac{U_f}{I_f} = \frac{\frac{U}{\sqrt{3}}}{I_f} = \frac{200V}{12A} = \underline{\underline{9,62 \Omega}}$$

$$I = \frac{U}{Z_f + Z_f} = \frac{200V}{9,62\Omega + 9,62\Omega} = \underline{\underline{10,39 A}}$$

c) TREKANTKOPLING:


$$I_f = \frac{U_f}{Z_f} = \frac{200V}{9,62\Omega} = \underline{\underline{20,78 A}}$$

$$I = I_f \cdot \sqrt{3} = 20,78A \cdot \sqrt{3} = \underline{\underline{36 A}}$$

$$S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 200V \cdot 36A = \underline{\underline{12470,8 VA}}$$

$$\bar{S} = S \angle \varphi = 12470,8VA \angle 31,79^\circ = \underline{\underline{10560W + j6570VAR}}$$

d)

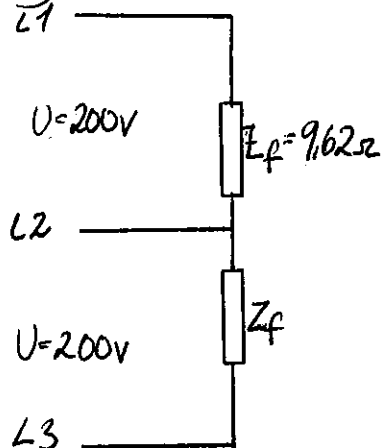


strømmen i fasene L1 og L3:

$$I_f = \frac{U_f}{Z_f} = \frac{200V}{9,62\Omega} = \underline{\underline{20,79 A}}$$

strømmen i fasen L2

$$I_f = I_f \cdot 2 = \underline{\underline{41,58 A}}$$

8.1.9

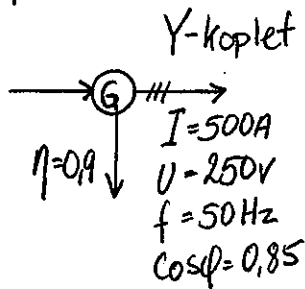

$$a) U_f = \frac{U}{\sqrt{3}} = \frac{250V}{\sqrt{3}} = \underline{\underline{144,3V}}$$

$$b) S = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 250V \cdot 500A = \underline{\underline{216,5 kVA}}$$

$$c) \cos\phi = 0,85 \Rightarrow \angle\phi = \underline{\underline{31,79^\circ}}$$

$$\vec{S} = S \angle\phi = 216,5 \cdot 10^3 VA \angle 31,79^\circ = \underline{\underline{184,0 kW + j 114,0 kVAR}}$$

$$d) P_{tlf} = P_{avg} + \Delta P = 184,0 \cdot 10^3 W + 12,0 \cdot 10^3 W = \underline{\underline{196,0 kW}}$$

$$\eta = \frac{P_{avg}}{P_{tlf}} = \frac{184,0 \cdot 10^3 W}{196,0 \cdot 10^3 W} = \underline{\underline{0,939}}$$